

ENGR 2420: Lab 3 Prelab Solution

October 8, 2020

Prelab

1. Forward-Active Bipolar Transistor Characteristics.

- (a) We know that $I_e = I_c/\alpha$, that $I_b = I_c/\beta$, and that $I_e = I_c + I_b$. By substituting the two former relations into the third, we have that

$$\begin{aligned} I_e &= I_c + I_b \\ \frac{I_c}{\alpha} &= I_c + \frac{I_c}{\beta} \\ \frac{I_c}{\alpha} &= \left(1 + \frac{1}{\beta}\right) I_c \\ \frac{1}{\alpha} &= \frac{1 + \beta}{\beta} \\ \alpha &= \frac{\beta}{1 + \beta}. \end{aligned}$$

Alternatively, we can solve this equation for β , thereby obtaining

$$\begin{aligned} \frac{1}{\beta} &= \frac{1}{\alpha} - 1 \\ \frac{1}{\beta} &= \frac{1 - \alpha}{\alpha} \\ \beta &= \frac{\alpha}{1 - \alpha}. \end{aligned}$$

- (b) We know that the base current related to the base and emitter voltages through

$$I_b = \frac{I_s}{\beta} \cdot e^{(V_b - V_e)/U_T}.$$

We can invert this relationship, thereby obtaining

$$V_b = V_e + U_T \log \frac{\beta I_b}{I_s},$$

which we can differentiate with respect to I_b to obtain the incremental resistance of the base terminal, r_b , which is given by

$$r_b = \frac{\partial V_b}{\partial I_b} = 0 + U_T \cdot \frac{1}{\beta I_b / I_s} \cdot \frac{\beta}{I_s} = \frac{U_T}{I_b}.$$

- (c) We know that the collector current is related to the base and emitter voltages through

$$I_c = I_s e^{(V_b - V_e)/U_T},$$

which we can differentiate with respect to V_b to obtain an expression for the incremental transconductance gain, g_m , of the bipolar transistor. Doing so, we have that

$$g_m = \frac{\partial I_c}{\partial V_b} = \underbrace{I_s e^{(V_b - V_e)/U_T}}_{I_c} \cdot \frac{1}{U_T} = \frac{I_c}{U_T}.$$

- (d) From part c, we know that

$$r_b = \frac{U_T}{I_b} = \beta \cdot \frac{U_T}{\beta I_b} = \beta \cdot \frac{U_T}{I_c} = \frac{\beta}{g_m}.$$

2. Emitter-Degenerated Bipolar Transistor.

- (a) From Section 3.3 of the bipolar transistor handout, we know have that the incremental resistance of the base terminal of a bipolar transistor whose emitter is degenerated by a resistor, R , is given by

$$R_b = r_b + (\beta + 1) R = \frac{U_T}{I_b} + (\beta + 1) R \approx \frac{U_T}{I_b} + \beta R = \beta R \left(1 + \frac{U_T}{\beta I_b R} \right),$$

where the approximation follows if $\beta \gg 1$.

- (b) From Section 3.3 of the bipolar transistor handout, we also know that the incremental transconductance gain of the bipolar transistor whose emitter is degenerated by a resistor, R , is given by

$$\begin{aligned} G_m &= \frac{g_m}{1 + R/r_e} \\ &= \frac{g_m}{1 + g_m R / \alpha} \\ &= \frac{\alpha}{R} \cdot \frac{1}{1 + \alpha / g_m R} \\ &= \frac{\alpha}{R} \cdot \frac{1}{1 + \alpha U_T / I_c R} \\ &\approx \frac{1}{R} \cdot \frac{1}{1 + U_T / I_c R}, \end{aligned}$$

where the approximation follows if $\alpha \approx 1$, which from part a of question 1 is true if $\beta \gg 1$.

- (c) Before we make the change in V_b by δV_b , we know by KCL that the emitter current is given both by

$$I_e = \frac{I_s}{\alpha} \cdot e^{(V_b - V_e)/U_T},$$

and by

$$I_e = \frac{V_e}{R}.$$

The change in V_b results in a change in I_e by δI_e and in V_e by δV_e . After the change, we can thus express the emitter current using the transistor characteristic as

$$\begin{aligned} I_e + \delta I_e &= \frac{I_s}{\alpha} \cdot e^{((V_b + \delta V_b) - (V_e + \delta V_e))/U_T} \\ &= \frac{I_s}{\alpha} \cdot e^{(V_b - V_e)/U_T} \cdot e^{(\delta V_b - \delta V_e)/U_T} \\ &= I_e e^{(\delta V_b - \delta V_e)/U_T} \\ &\approx I_e \left(1 + \frac{\delta V_b - \delta V_e}{U_T} \right) \\ &= I_e + \frac{\delta V_b - \delta V_e}{U_T/I_e}, \end{aligned}$$

where the approximation follows if $|\delta V_b - \delta V_e| \ll U_T$, by expanding the exponential in a Taylor series and truncating after the linear term. By subtracting I_e from both sides of this equation, we obtain an expression for δI_e , given by

$$\delta I_e = \frac{\delta V_b - \delta V_e}{U_T/I_e}.$$

Likewise, we can express the emitter current after the change using Ohm's law as

$$I_e + \delta I_e = \frac{V_e + \delta V_e}{R} = \underbrace{\frac{V_e}{R}}_{I_e} + \frac{\delta V_e}{R}.$$

By subtracting I_e from both sides of this equation, we obtain a second expression for δI_e , given by

$$\delta I_e = \frac{\delta V_e}{R}.$$

By equating these two expressions for δI_e , we can solve for δV_e to find that

$$\delta V_e = \frac{I_e}{I_e + (U_T/R)} \cdot \delta V_b.$$

- (d) The change in V_e will be half the change in V_b when $I_e = U_T/R$. At this emitter current level, the collector current, which is I_{on} , is given by

$$I_{on} = \alpha \frac{U_T}{R} \approx \frac{U_T}{R},$$

where the approximation follows if $\alpha \approx 1$. Using this result, we can express our final result from part a in terms of I_{on} as

$$R_b \approx \beta R \left(1 + \frac{U_T}{\beta I_b R} \right) = \beta R \left(1 + \frac{I_{on}}{\beta I_b} \right).$$

Likewise, we can express our final result from part b in terms of I_{on} as

$$G_m \approx \frac{1}{R} \cdot \frac{1}{1 + U_T/I_c R} = \frac{1}{R} \cdot \frac{1}{1 + I_{\text{on}}/I_c}.$$

(e) By using the transistor's characteristic, we can express V_{on} as

$$V_{\text{on}} = U_T \log \frac{I_{\text{on}}}{I_s}.$$

(f) By applying KCL at the emitter node, we have that

$$\begin{aligned} \frac{V_e}{R} &= \frac{I_s}{\alpha} \cdot e^{V_{\text{be}}/U_T} \\ 0 &= -V_e + R \cdot \frac{I_s}{\alpha} \cdot e^{V_{\text{be}}/U_T} \\ \frac{V_b}{U_T} &= \frac{V_b - V_e}{U_T} + \frac{I_s}{\alpha U_T / R} \cdot e^{V_{\text{be}}/U_T} \\ \frac{V_b}{U_T} &= \frac{V_{\text{be}}}{U_T} + \frac{I_s}{I_{\text{on}}} \cdot e^{V_{\text{be}}/U_T} \\ \frac{V_b}{U_T} &= \frac{V_{\text{be}}}{U_T} + e^{-V_{\text{on}}/U_T} e^{V_{\text{be}}/U_T} \\ \frac{V_b - V_{\text{on}}}{U_T} &= \frac{V_{\text{be}} - V_{\text{on}}}{U_T} + e^{(V_{\text{be}} - V_{\text{on}})/U_T}. \end{aligned}$$

(g) If $V_{\text{be}} < V_{\text{on}}$ by more than a few U_T , then it follows that

$$e^{(V_{\text{be}} - V_{\text{on}})/U_T} \ll \left| \frac{V_{\text{be}} - V_{\text{on}}}{U_T} \right|.$$

In this regime, we can approximate the result from part f as

$$\frac{V_b - V_{\text{on}}}{U_T} = \frac{V_{\text{be}} - V_{\text{on}}}{U_T} + e^{(V_{\text{be}} - V_{\text{on}})/U_T} \approx \frac{V_{\text{be}} - V_{\text{on}}}{U_T},$$

which implies that $V_e \approx 0$ and that

$$I_c = I_s e^{V_{\text{be}}/U_T} \approx I_s e^{V_b/U_T}.$$

(h) If $V_{\text{be}} > V_{\text{on}}$ by more than a few U_T , then it follows that

$$e^{(V_{\text{be}} - V_{\text{on}})/U_T} \gg \frac{V_{\text{be}} - V_{\text{on}}}{U_T}.$$

In this regime, we can approximate the result from part f as

$$\frac{V_b - V_{\text{on}}}{U_T} = \frac{V_{\text{be}} - V_{\text{on}}}{U_T} + e^{(V_{\text{be}} - V_{\text{on}})/U_T} \approx e^{(V_{\text{be}} - V_{\text{on}})/U_T},$$

which implies that

$$\begin{aligned} e^{V_{be}/U_T} &\approx e^{V_{on}/U_T} \cdot \frac{V_b - V_{on}}{U_T} \\ &= \alpha \cdot \frac{U_T}{RI_s} \cdot \frac{V_b - V_{on}}{U_T} \\ &= \frac{\alpha}{I_s} \cdot \frac{V_b - V_{on}}{R}. \end{aligned}$$

The collector current is then given by

$$I_c = I_s e^{V_{be}/U_T} \approx I_s \cdot \frac{\alpha}{I_s} \cdot \frac{V_b - V_{on}}{R} = \alpha \cdot \frac{V_b - V_{on}}{R} \approx \frac{V_b - V_{on}}{R},$$

where the approximation follows from the fact that $\alpha \approx 1$.