

Lab 3: Resistors and Diodes

ENGR 2420 | Olin College

Jasper Katzban

October 10, 2020

Prelab

1. Forward-Active Bipolar Transistor Characteristics

- (a) We have equations relating both α and β to I_s , so we can setup an equation and simplify as shown.

$$\frac{I_b \beta}{e^{V_{be}/U_T}} = \frac{I_e \alpha}{e^{V_{be}/U_T}}$$
$$I_b \beta = I_e \alpha$$

- (b) From the lab handout, we're given a derivation for r_d in terms of I_b as shown:

$$r_b = \frac{\delta V_b}{\delta I_b}$$
$$r_b = \left(\frac{I_s}{\beta} \cdot e^{V_{be}/U_T} \cdot \frac{1}{U_T} \right)^{-1}$$
$$r_d = \frac{U_T}{I_b}$$

- (c) We can find an expression for g_m in terms of I_c as follows.

$$g_m = \frac{\delta I_c}{\delta V_b}$$
$$g_m = I_s e^{\frac{V_{be}}{U_T}} \frac{1}{U_T}$$
$$g_m = \frac{I_c}{U_T}$$

- (d) r_d and g_m are inversely proportional to each other as a function of β , as shown.

$$g_m \frac{e^{\frac{V_b}{V_e}}}{U_T} \rightarrow \frac{I_c}{U_T} \rightarrow \frac{\beta I_b}{U_T}$$
$$r_d = \frac{U_T}{I_b}, g_m = \frac{\beta I_b}{U_T}$$
$$r_d = \frac{\beta}{g_m}$$

2. Emitter-Degenerated Bipolar Transistor

(a) We can represent r_b in terms of I as shown.

$$\begin{aligned} R_b &= \frac{\delta V_b}{\delta I_b} = r_b + (\beta_F + 1) \cdot R_x \\ r_b &= R_b - (\beta_F + 1) \cdot R_x \\ r_b &= R_b - \left(\frac{I_s}{I_b} e^{\frac{V_{be}}{U_T}} + 1 \right) \cdot R_x \end{aligned}$$

(b) We can derive an equation for G_m in terms of I_e as follows:

$$\begin{aligned} G_m &= \frac{\delta I_e}{\delta V_b} \\ G_m &= \frac{g_m}{1 + R_x/r_e} \\ G_m &= \frac{g_m}{1 + R_x/\frac{r_b}{\beta_F + 1}} \\ G_m &= g_m \left(1 + R_x \frac{R_b - \frac{I_s}{I_b} e^{V_{be}/U_T}}{\frac{I_s}{I_b} e^{V_{be}/U_T} + 1} \right)^{-1} \end{aligned}$$

(c) We can represent δV_e in terms of δV_b as follows:

$$\begin{aligned} I_e + \delta I_e &= \frac{I_s}{\alpha} \cdot e^{\frac{V_{be}}{U_T}} \cdot e^{\frac{\delta V_b - \delta V_e}{U_T}} \\ I_e + \delta I_e &= \frac{I_s}{\alpha} \cdot e^{\frac{V_{be}}{U_T}} \left(1 + \frac{\delta V_b - \delta V_e}{U_T} \right) \\ I_e + \delta I_e &= I_e \cdot \left(1 + \frac{\delta V_b - \delta V_e}{U_T} \right) \\ I_e + \delta I_e &= I_e + I_e \cdot \left(\frac{\delta V_b - \delta V_e}{U_T} \right) \\ \delta I_e &= I_e \cdot \left(\frac{\delta V_b - \delta V_e}{U_T} \right) \\ \frac{\delta V_e}{R} &= I_e \cdot \left(\frac{\delta V_b - \delta V_e}{U_T} \right) \\ \delta V_e U_T &= R \cdot I_e \cdot (\delta V_b - \delta V_e) \\ \delta V_e &= \frac{\delta R V_b I_e}{U_T + R I_e} \\ \delta V_e &= \frac{\delta V_b I_e}{\frac{U_T}{R} + I_e} \end{aligned}$$

(d) We can represent I_{on} as a function of R as follows:

$$\begin{aligned} \delta V_b &= \delta I_b \cdot \frac{U_T \beta}{I_{on}} + \frac{1}{2} \delta V_b \\ \frac{1}{2} (\delta I_b \frac{U_T \beta}{I_{on}} + \delta I_b \cdot (\beta + 1) \cdot R) &= \frac{\delta I_b U_T \beta}{I_{on}} \\ \frac{1}{2} \left(\frac{U_T \beta}{I_{on}} + (\beta + 1) \cdot R \right) &= \frac{U_T \beta}{I_{on}} \\ \frac{1}{2} \left(\frac{U_T \beta}{I_{on}} \right) + \frac{1}{2} R (\beta + 1) &= \frac{U_T \beta}{I_{on}} \\ R (\beta + 1) &= \frac{U_T \beta}{I_{on}} \\ I_{on} &= \frac{U_T \alpha}{R} \end{aligned}$$

(e) We can simplify an expression for V_{on} as a function of I_{on} as follows.

$$I = I_{on} = I_s e^{V/U_T} - 1$$

$$V_{on} = U_T \log \frac{I_{on}}{I_s} + 1$$

(f) We can express the relationship between I_c and V_b in terms of V_{on} and U_T .

$$\frac{V_e}{R} = I_c + \frac{I_c}{\beta}$$

$$\frac{V_b - V_{be}}{R} = I_c + \frac{I_c}{\beta}$$

$$I_{on} \frac{V_b - V_{be}}{U_T \cdot \alpha} = I_c + \frac{I_c}{\beta}$$

$$I_s \cdot e^{\frac{V_{on}}{U_T}} \cdot \frac{V_b - V_{be}}{U_T \cdot \alpha} = I_c \left(1 + \frac{1}{\beta}\right)$$

$$I_s e^{\frac{V_{on}}{U_T}} \cdot \frac{V_b}{V_{be}} = I_s e^{\frac{V_{be}}{U_T}} \cdot \frac{1}{\alpha}$$

$$e^{\frac{V_{on}}{U_T}} \cdot \frac{V_b}{V_{be}} = e^{\frac{V_{be}}{U_T}} \cdot \frac{1}{\alpha}$$

$$e^{\frac{V_{on}}{U_T}} \cdot \frac{V_b}{V_{be}} = U_T e^{\frac{V_{be}}{U_T}}$$

$$V_b - V_{be} = U_T e^{\frac{V_{be} - V_{on}}{U_T}}$$

$$V_b = U_T + V_{be} + U_T e^{\frac{V_{be} - V_{on}}{U_T}}$$

$$V_b = V_{be} \frac{I_c}{g_m} e^{\frac{V_{be} - V_{on}}{U_T}}$$

$$V_b - V_{on} = V_{be} - V_{on} + \frac{I_c}{g_m} e^{\frac{V_{be} - V_{on}}{U_T}}$$

(g) We can approximate the previous relationship when $V_{be} < V_{on}$ as $V_b = V_{be}$ because as V_{on} approaches a large number (infinity), the entire exponential term above will go to zero because e will be raised to a negative power.

Because we factor out the term containing I_c , we can't generate an expression relating it to V_b . This makes sense because the transistor should effectively not pass a current to the collector when the V_{be} is less than the turn on voltage.

(h) We can approximate the relationship when $V_{be} > V_{on}$ as $V_b = V_{be} + \frac{I_c}{g_m} e^{\frac{V_{be}}{U_T}}$
Solving for I_c , we get the following:

$$V_b = V_{be} + \frac{I_c}{g_m} e^{\frac{V_{be}}{U_T}}$$

$$V_b - V_{be} = \frac{I_c}{g_m} e^{\frac{V_{be}}{U_T}}$$

$$g_m (V_b - V_{be}) = I_c e^{\frac{V_{be}}{U_T}}$$

$$g_m \frac{V_b - V_{be}}{e^{\frac{V_{be}}{U_T}}} = I_c$$