

# Lab 1: Resistors and Resistive Networks

ENGR 2420 | Olin College


Jasper Katzban

September 17, 2020


## Prelab

### 1. Electrical Measurement Concepts

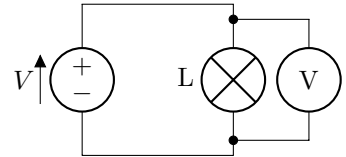- (a) An ideal voltage meter has **infinite** internal resistance and should be connected in **parallel** with the circuit or device being tested.



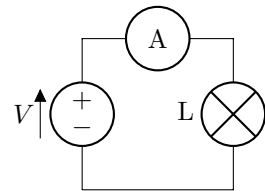- (b) An ideal current meter has **zero** internal resistance and should be connected in **series** with the circuit or device being tested.



### 2. Resistive Divider Accuracy

To find the coefficient of variation,  $CV$ , of a resistive divider, we start with the gain equation from a resistor divider.

$$A = \frac{R_2}{R_1 + R_2}$$

and plug it into the sensitivity equation like so.

$$S_{R_i}^A = R_i \frac{\delta \ln \frac{R_2}{R_1 + R_2}}{\delta R_i}$$

Solving for the sensitivity with each resistor gives

$$S_{R_1}^A = \frac{-R_1}{R_1 + R_2} \text{ and } S_{R_2}^A = 1 - \frac{R_2}{R_1 + R_2}.$$

Now, we'll use this equation

$$CV_A = \sqrt{\sum_{i=1}^n (S_{R_i}^A)^2 \cdot (CV_{R_i})^2}$$

and substitute in our resistor values and sensitivities like so.

$$CV_A = \sqrt{\left(\frac{-R_1}{R_1 + R_2}\right)^2 \cdot CV_{R_1}^2 + \left(1 - \frac{R_2}{R_1 + R_2}\right)^2 \cdot CV_{R_2}^2}$$

Simplifying, this gives us a final expression for the coefficient of variation as the following:

$$CV_A = \frac{R_1 \sqrt{CV_1^2 + CV_2^2}}{R_1 + R_2}$$

### 3. R-2R Ladder Network

One interesting attribute of the  $R$ - $2R$  ladder network is that at each node before a branch, the resistance of the remainder of the ladder from that point is simply  $2R$ .

Furthermore, at each branch the current,  $I_n$ , halves since it's being divided between the branch and the rest of the ladder

Incorporating this information into  $I = \frac{V}{R}$ , we can quantify the sum of the current in the whole ladder as the following equation:

$$I_n = \frac{V}{2^{n+1} \cdot R}$$


Therefore, the currents flowing through each of the  $2R$  branches as a function of  $V$  and  $R$  are as follows:

$$I_1 = \frac{V}{4 \cdot R} \quad I_n = \frac{V}{2^{n+1} \cdot R} \quad I_{N-1} = \frac{V}{R} \quad I_N = \frac{V}{2^{N+1} \cdot R}$$
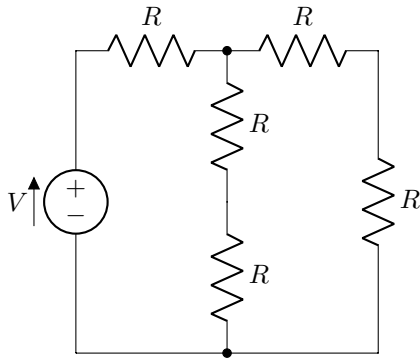
### 4. Accurate 2:1 Resistor Ratios

Two different implementations of a single unit in an  $R$ - $2R$  ladder network are shown below.

This implementation uses 3 resistors for a single intermediary ladder branch and an additional 2 for the final branch, for a minimum of **5 resistors** in the smallest possible  $R$ - $2R$  ladder.



This implementation uses less resistors, with 3 for a single intermediary ladder branch and only one additional resistor for the final branch, for a minimum of **4 resistors** in the smallest possible  $R$ - $2R$  ladder.

