

# INTRODUCTION TO LTSPICE

## Objectives

In this assignment, you will go through the process of constructing a schematic in LTspice, performing a DC sweep simulation, and creating a pdf file with figures showing the LTspice schematic and the simulation results with curve fits.

## Background


Fig. 1a shows the schematic of an *inverting amplifier* circuit made from an op amp and two resistors. The circuit's input voltage couples into the op amp's inverting input through  $R_1$ , and the op amp's output voltage is fed back into the inverting input through a  $R_2$ . The op amp's noninverting input is held at a reference voltage,  $V_{\text{ref}}$ , somewhere within the power supply rails. The op amp adjusts  $V_{\text{out}}$  so that  $V$  becomes or remains equal to  $V_{\text{ref}}$ . A change in  $V_{\text{in}}$  has a tendency to change  $V$  in the same direction. To compensate, the op amp changes its output in the opposite direction so that  $V$  remains constant or returns to  $V_{\text{ref}}$ . The amount by which  $V_{\text{out}}$  must change to compensate a given change in  $V_{\text{in}}$  is set by the ratio of the two resistors—the circuit can either amplify, invert (i.e., have a gain of  $-1$ ), or attenuate, depending on the size of  $R_2$  compared to  $R_1$ . Fig. 1b show the inverting amplifier's voltage transfer characteristic (VTC) for two values of  $V_{\text{ref}}$ . Until  $V_{\text{out}}$  saturates at one of the rails, the inverting amplifier's VTC is given by

$$V_{\text{out}} = V_{\text{ref}} + A(V_{\text{in}} - V_{\text{ref}}),$$

where the gain is  $A = -R_2/R_1$ .

## Experiment

Construct an inverting amplifier schematic in LTspice with a nominal gain of  $-2$ . Power your circuit from a single-ended  $+5\text{ V}$  power supply. Perform a DC sweep simulation of your circuit's VTC for three values of  $V_{\text{ref}}$ . In your report, include a figure showing your LTspice schematic. Also include a single plot showing all three VTCs along with linear fits to the parts of the VTCs where the op amp's output is not saturated at one of the rails. For your plot, you should show the simulation results as discrete pointmarkers and you should show the fits as lines. You should adjust the axes limits so that the simulation results take up most of the plot. You should label your axes including appropriate units. Include the voltage gains that you obtain for each VTC from the slope of the best fit line. Please use vector-based graphics formats instead of raster-based ones.

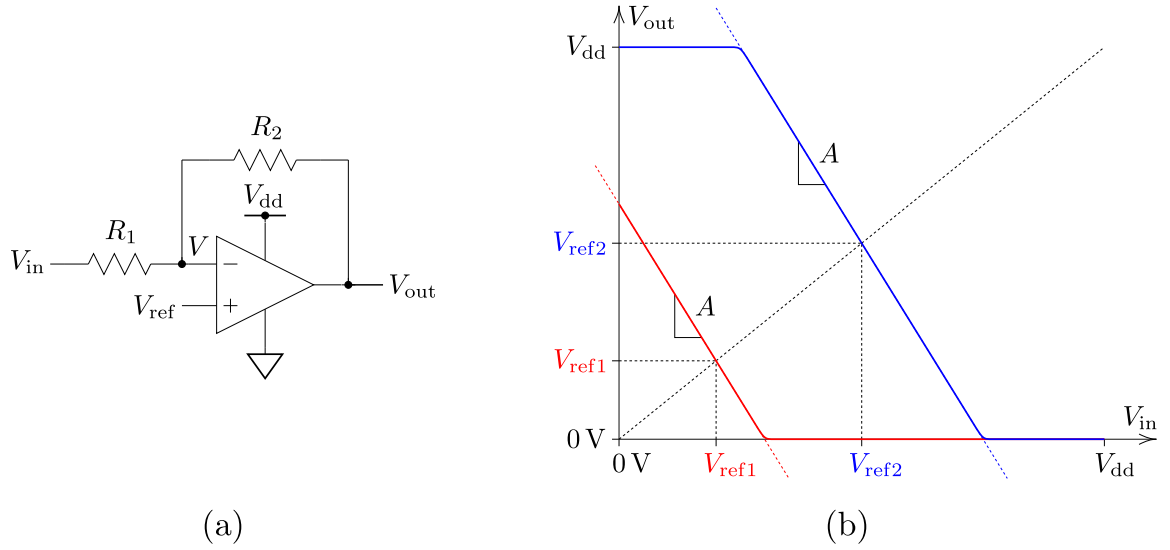

**Figure 1:** Inverting amplifier (a) circuit schematic and (b) voltage transfer characterisite (VTC) for two values of  $V_{ref}$ .

## Deliverable

A single pdf file containing your name and the two figures described uploaded to Canvas by noon on Wednesday, September 16, 2020.