

Lab 2: Resistors and Diodes

ENGR 2420 | Olin College

Jasper Katzban

September 25, 2020

Prelab

1. Diode-Connected Transistor Characteristics

- (a) If we force a current greater than a nanoamp into the diode-connected transistor, we could represent its characteristics with the following equation.

$$\begin{aligned}2nA &= 3fA \cdot e^{\frac{V}{U_T}} - 1 \\ \frac{2 \times 10^{-9}A}{2 \times 10^{-15}A} &= e^{\frac{V}{U_T}} - 1 \\ 1000000A &= e^{\frac{V}{U_T}} - 1 \\ 1000000 + 1 &= e^{\frac{V}{U_T}}\end{aligned}$$

When we simplify, we see that the term, $+1$, does not have much of an influence given that I_s is so small. Therefore we can conclude that the equation $I = I_s(e^{\frac{V}{U_T}})$ a good approximation of the transistor's characteristics. We'll use it for the remainder of the questions in this part of the lab.

- (b) In general, an increase of I by a factor n yields a voltage generalized by $V = U_T \ln(n) + U_T \ln(\frac{I}{I_s})$.

Increasing the current by e fold gives:

$$\begin{aligned}V &= U_T(\ln(e \cdot I) - \ln I_s) \\ &\quad \downarrow \\ V &= U_T \ln e + U_T \ln \frac{I}{I_s} \\ &\quad \downarrow \\ V &= U_T + U_T \ln \frac{I}{I_s}\end{aligned}$$

Increasing the current by a decade yields:

$$\begin{aligned}V &= U_T(\ln(10 \cdot I) - \ln I_s) \\ &\quad \downarrow \\ V &= U_T \ln(10) + U_T \ln \frac{I}{I_s}\end{aligned}$$

- (c) The equation for *incremental diode resistance* can be simplified as show.

$$r_d = \frac{\delta V}{\delta I} = \frac{\delta}{\delta I}(U_T \ln I - U_T \ln I_s) = \frac{U_T}{I}$$

- (d) Given what we've established above, a voltage across the transistor would result in the same behavior since V and I are linked in the approximated ideal diode equation, $I = I_s(e^{\frac{V}{U_T}})$.
- (e) To start, we can take the approximated ideal diode equation, $I = I_s e^{\frac{V}{U_T}}$, and take the natural log of both sides as shown.

$$\ln I = \ln e^{\frac{V}{U_T}} + \ln I_s$$

If we plot the above on a semilog-y plot, we effectively have an equation in $y = mx + b$ form, which makes the above analogous to the following.

$$V(I) = \frac{I}{U_T} + I_s$$

We can now compute linear regression on the data, extracting U_T from the slope of the best fit line and I_s as its intercept.

2. Characteristics of a Resistor and a Diode in Series

- (a) Equations for the voltage across each component are as follows.

$$\begin{aligned} V_R &= IR \\ V_T &= U_T \ln\left(\frac{I}{I_s}\right) \\ V_{in} &= IR + U_T \ln\left(\frac{I}{I_s}\right) \end{aligned}$$

- (b) Equations for the change in voltage across each component are as follows.

$$\begin{aligned} \delta V_R &= \frac{\delta}{\delta I}(IR) = R \\ \delta V_T &= \frac{\delta}{\delta I}(U_T \ln\left(\frac{I}{I_s}\right)) = \frac{U_T}{I} \\ \delta V_{in} &= \frac{\delta}{\delta I}(U_T \ln\left(\frac{I}{I_s}\right) + IR) = \frac{U_T}{I} + R \end{aligned}$$

- (c) The derived equation for the *turn on current* of the transistor as a function of R is as follows.

$$I_{on} = \frac{U_T}{R}$$

- (d) We can express V_{on} as the following equation.

$$V_{on} = U_T \ln\left(\frac{I_{on}}{I_s}\right)$$

- (e) We can represent the fractions of δV_{in} that appear across the transistor and resistor as follows.

$$\begin{aligned} \frac{\delta V_T}{\delta V_{in}} &= \frac{\frac{U_T}{I}}{\frac{U_T}{I} + R} & \frac{\delta V_R}{\delta V_{in}} &= \frac{R}{\frac{U_T}{I} + R} \\ &\downarrow & &\downarrow \\ \frac{\delta V_T}{\delta V_{in}} &= \frac{I_{on}}{I_{on} + I} & \frac{\delta V_R}{\delta V_{in}} &= 1 - \frac{I_{on}}{I_{on} + I} \end{aligned}$$

- (f)
- When $I \ll I_{on}$, δV_T , almost all of δV_{in} is coming from δV_T .
 - V_{in} will change logarithmically with respect to I
 - When $I \gg I_{on}$, δV_T , contributes a nothing to δV_{in}
 - V_T is not changing much with respect to V_{in}
 - V_{in} changes linearly with respect to I
- (g)
- V would change linearly with V_{in} when $V_{in} < V_{on}$ by more than a few U_T
 - I does not depend on V_{in} in these circumstances given the current response of the transistor
 - V would change exponentially with V_{in} when $V_{in} > V_{on}$ by more than a few U_T
 - I would correlate exponentially with V_{in}